



**Curtis Robinson | Mack Atencia**


**ELEN 100 Lab**

**February 17, 2023**

**Project 1 Lab Report**

## Problem 1:

### Transfer Function Calculation:

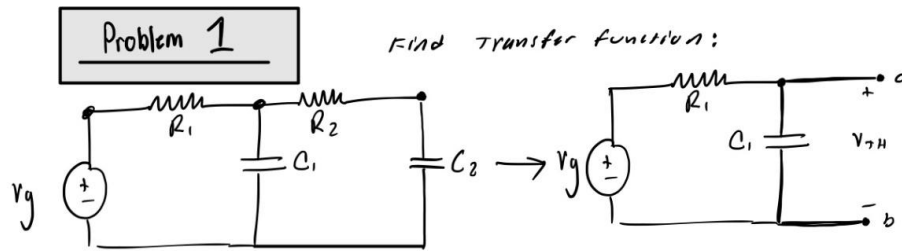


#### Voltage Divider:

$$V_{TH} = \frac{V_g (C_1)}{R_1 + C_1} \rightarrow V_{TH} = (V_g) \frac{\frac{1}{j\omega C_1}}{R_1 + \frac{1}{j\omega C_1}}$$

$$\Rightarrow \frac{\frac{1}{j\omega C_1}}{\frac{R_1 j\omega C_1}{j\omega C_1} + \frac{1}{j\omega C_1}} \Rightarrow \frac{\frac{1}{j\omega C_1}}{\frac{1 + R_1 j\omega C_1}{j\omega C_1}}$$


$$\Rightarrow (1 + R_1 j\omega C_1) V_g = V_{TH}$$

#### Thevenin Circuit

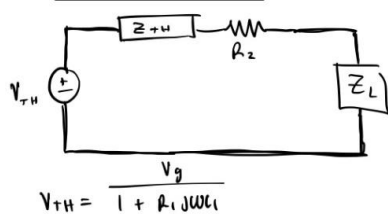

#### Z<sub>TH</sub>

Parallel components  
 $a || b = \frac{a \cdot b}{a + b}$

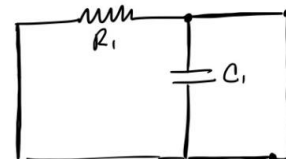


$$Z_{TH} = R_1 || C_1$$

$$= \frac{(R_1) \left( \frac{1}{j\omega C_1} \right)}{R_1 + \frac{1}{j\omega C_1}}$$

$$Z_{TH} = \frac{R_1 / j\omega C_1}{R_1 + \frac{1}{j\omega C_1}}$$

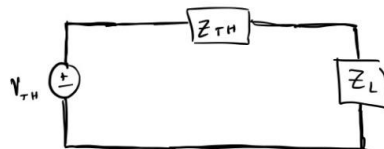
#### Thevenin Circuit w/ R<sub>2</sub> combined



$$Z_{TH} = Z_{TH} + R_2$$

$$Z_{TH} = \frac{R_1 + R_2 + j\omega C_1 R_1 R_2}{1 + j\omega C_1 R_1}$$

# Problem 1 continued...

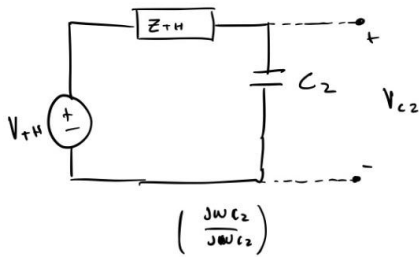

$$= \frac{R_1 + R_2 + j\omega L_1 R_1 R_2}{1 + j\omega L_1 R_1} + \frac{1}{j\omega C_2} \left( \frac{1 + j\omega L_1 R_1}{1 + j\omega L_1 R_1} \right)$$

$$= \frac{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2)}{(j\omega C_2)(1 + j\omega L_1 R_1)} + \frac{1 + j\omega L_1 R_1}{(j\omega C_2)(1 + j\omega L_1 R_1)}$$

$$\frac{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)}{(j\omega C_2)(1 + j\omega L_1 R_1)}$$

## Voltage Divider:

$$Z_{TH} = \frac{R_1 + R_2 + j\omega L_1 R_1 R_2}{1 + j\omega L_1 R_1}$$

$$V_{C2} = \frac{\frac{R_1 + R_2 + j\omega L_1 R_1 R_2}{1 + j\omega L_1 R_1}}{\frac{R_1 + R_2 + j\omega L_1 R_1 R_2}{1 + j\omega L_1 R_1} + \frac{1}{j\omega C_2}} \cdot V_{TH}$$

$$= \frac{\frac{1}{j\omega C_2}}{\frac{R_1 + R_2 + j\omega L_1 R_1 R_2}{1 + j\omega L_1 R_1} + \frac{1}{j\omega C_2}} \cdot \frac{V_g}{1 + R_1 j\omega L_1}$$

$$= \frac{\frac{1}{j\omega C_2}}{\frac{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)}{(j\omega C_2)(1 + j\omega L_1 R_1)}} \cdot \frac{V_g}{1 + R_1 j\omega L_1}$$

$$V_{C2} = \frac{\cancel{j\omega C_2} (1 + j\omega L_1 R_1)}{\cancel{j\omega C_2} [(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)]} \cdot \frac{V_g}{1 + R_1 j\omega L_1}$$

$$V_{C2} = \frac{(1 + j\omega L_1 R_1)}{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)} \cdot \frac{V_g}{1 + R_1 j\omega L_1}$$

$$V_{C2} = \frac{V_g}{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)}$$

$$\frac{V_{C2}}{V_g} = \frac{1}{(j\omega C_2)(R_1 + R_2 + j\omega L_1 R_1 R_2) + (1 + j\omega L_1 R_1)}$$

$$\frac{V_{C2}}{V_g} = \frac{1}{(R_1 j\omega C_2 + R_2 j\omega C_2 + j\omega C_1 R_1 R_2 j\omega C_2) + (1 + j\omega L_1 R_1)}$$

$$= \frac{1}{R_1 j\omega C_2 + R_2 j\omega C_2 + j\omega C_1 R_1 R_2 j\omega C_2 + 1 + j\omega L_1 R_1}$$

$$\frac{V_{C2}}{V_g} = \frac{1}{j\omega (R_1 C_2 + R_2 C_2 + j\omega C_1 R_1 R_2 C_2 + L_1 R_1) + 1}$$

$$j\omega R_1 C_2 + j\omega R_2 C_2 + (j\omega)^2 C_1 C_2 R_1 R_2 + j\omega L_1 R_1 + 1$$

$$H(j\omega) = \frac{V_{C2}}{V_g} = \frac{1}{1 + j\omega (R_1 C_2 + R_2 C_2 + L_1 R_1) + (j\omega)^2 C_1 R_1 R_2 C_2}$$

## Problem 2:

### Resistor Value Calculations:

#### Problem #2

$$\frac{V_{C2}}{V} = \frac{1}{j\omega(R_1C_2 + R_1C_1 + R_2C_2) + j\omega^2(C_1C_2R_1R_2) + 1}$$

$$\frac{1}{b} + \frac{1}{a} = R_1C_2 + R_1C_1 + R_2C_2$$

$$\frac{3000 + 20000}{3000 \cdot 20000} = R_1C_2 + R_1C_1 + R_2C_2$$

$$\frac{23}{60000} = R_1C_2 + R_1C_1 + R_2C_2$$

$$= R_1C_1 + R_1C_1 + R_2C_1$$

$$= C_1(R_1 + R_1 + R_2)$$

$$\frac{23}{60000} = C_1(2R_1 + R_2)$$

$$\frac{1}{ab} = C_1C_2R_1R_2$$

$$\frac{1}{3000 \cdot 20000} = (10^{-6})^2 R_1R_2$$

$$R_1 = \frac{1}{3000 \cdot 20000 \cdot (10^{-6})^2 \cdot R_2}$$

$$R_1 = 16666.67 \cdot \frac{1}{R_2}$$

$$\frac{23}{60000} = 10^{-6} \left( \frac{2 \cdot 16666.67}{R_2} + R_2 \right)$$

$$\frac{23}{60000} = \frac{.033}{R_2} + (R_2 \times 10^{-6})$$

$$\frac{23}{60000} \cdot R_2 = .033 + (R_2^2 \times 10^{-6})$$

$$0 = (10^{-6})R_2^2 - \left(\frac{23}{60000}\right)R_2 + (0.033)$$

All components

$$C_1 = C_2 = 10^{-6} \text{ F}$$

$$R_1 = 65.93 \text{ } \Omega$$

$$R_2 = 252.79 \text{ } \Omega$$

$$R_2 = 252.79 \text{ } \Omega ; 130.54 \text{ } \Omega$$


$$R_1 = 65.93 \text{ } \Omega ; 127.67 \text{ } \Omega$$

### Problem 3:

Nodal Analysis for MATLAB Matrix input:

Problem #3

NODE voltage  
circuit:

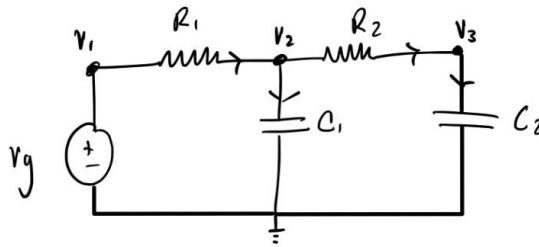

$$V_1) V_1 = V_g$$

$$V_2) -\frac{(V_1 - V_2)}{R_1} + \frac{(V_2 - 0)}{C_1} + \frac{(V_2 - V_3)}{R_2} = 0$$

$$V_3) -\frac{(V_2 - V_3)}{R_2} + \frac{(V_3 - 0)}{C_2} = 0$$

$$\rightarrow -\frac{V_1}{R_1} + \frac{V_2}{R_1} + \frac{V_2}{C_1} + \frac{V_2}{R_2} - \frac{V_3}{R_2} = 0$$

$$-\frac{V_2}{R_2} + \frac{V_3}{R_2} + \frac{V_3}{C_2} = 0$$

$$V_1 \left( -\frac{1}{R_1} \right) + V_2 \left( \frac{1}{R_1} + \frac{1}{C_1} + \frac{1}{R_2} \right) + V_3 \left( -\frac{1}{R_2} \right) = 0$$

$$V_2 \left( -\frac{1}{R_2} \right) + V_3 \left( \frac{1}{R_2} + \frac{1}{C_2} \right) = 0$$

$$-\frac{1}{R_1} \mid \frac{1}{R_1} + j\omega C_1 + \frac{1}{R_2} \mid -\frac{1}{R_2} \mid 0$$

$$-\frac{1}{R_2} \mid \frac{1}{R_2} + j\omega C_2 \mid 0$$

Final Matrix

$$\begin{pmatrix} 1 & 0 & 0 \\ -\frac{1}{R_1} & \frac{1}{R_1} + j\omega C_1 + \frac{1}{R_2} & -\frac{1}{R_2} \\ 0 & -\frac{1}{R_2} & \frac{1}{R_2} + j\omega C_2 \end{pmatrix} = \begin{pmatrix} V_1 \\ V_2 \\ V_3 \end{pmatrix} \begin{pmatrix} V_g \\ 0 \\ 0 \end{pmatrix}$$

\* matrix plugged into matlab

### MATLAB Script:

```
close all;
clear;
clc;

%Variable declarations
R1 = 65.93;
R2 = 252.79;
C1 = 10^-6;
C2 = 10^-6;


%Matrix declarations
G = [1, 0, 0; (-1/R1), (1/R1+1/R2), -1/R2; 0, (-1/R2), (1/R2)];
C = [0, 0, 0; 0, (C1), 0; 0, 0, C2];
b = [1; 0; 0];

%Varying frequencies
r = [1 2 3 4 5 6 7 8 9];
w = [r, (10*r), (1e2*r), (1e3*r), (1e4*r), (1e5*r)];
freq = (w/(2*pi));


%Calling graphing functions with the parameters
semilogx(freq, freqresp4(G, C, b, w))
grid
ylim([-100, 10]);
ylabel('20log|H(jw)|');
xlabel('w (rad/sec)');

hold on
```

### MATLAB Simulation Result:

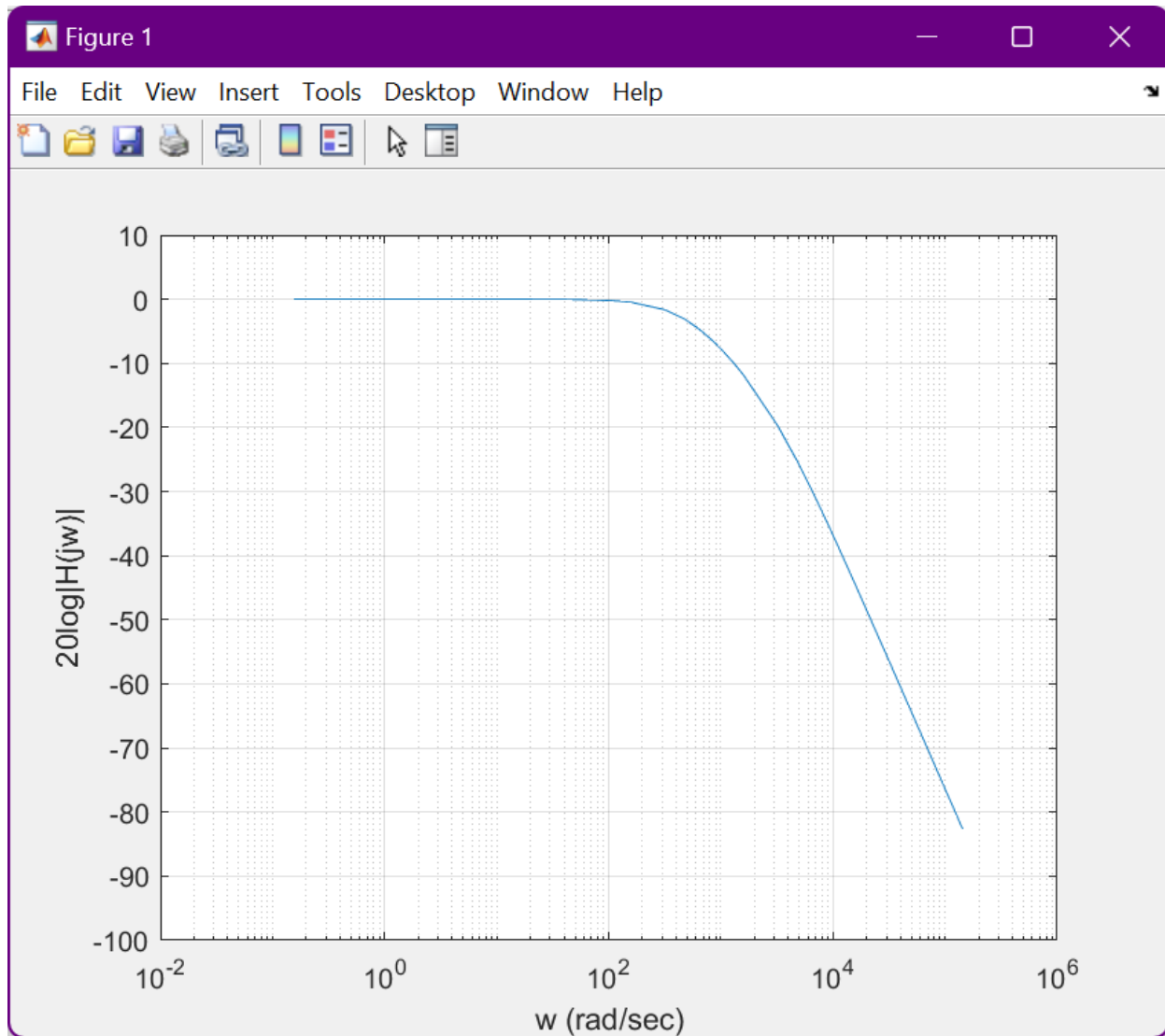


## MATLAB Run-time Results:

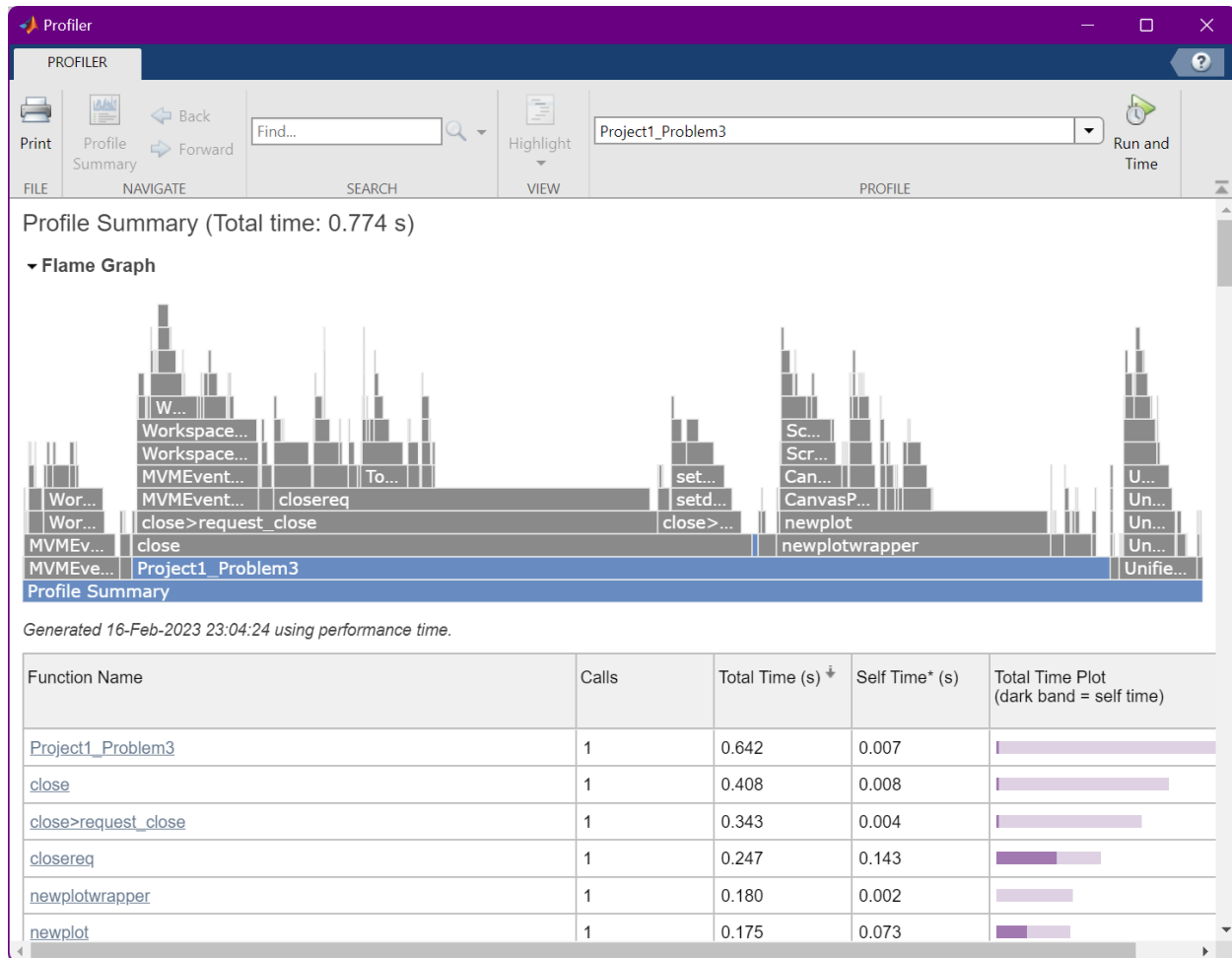



#### Problem 4:

##### SPICE Simulation Results:

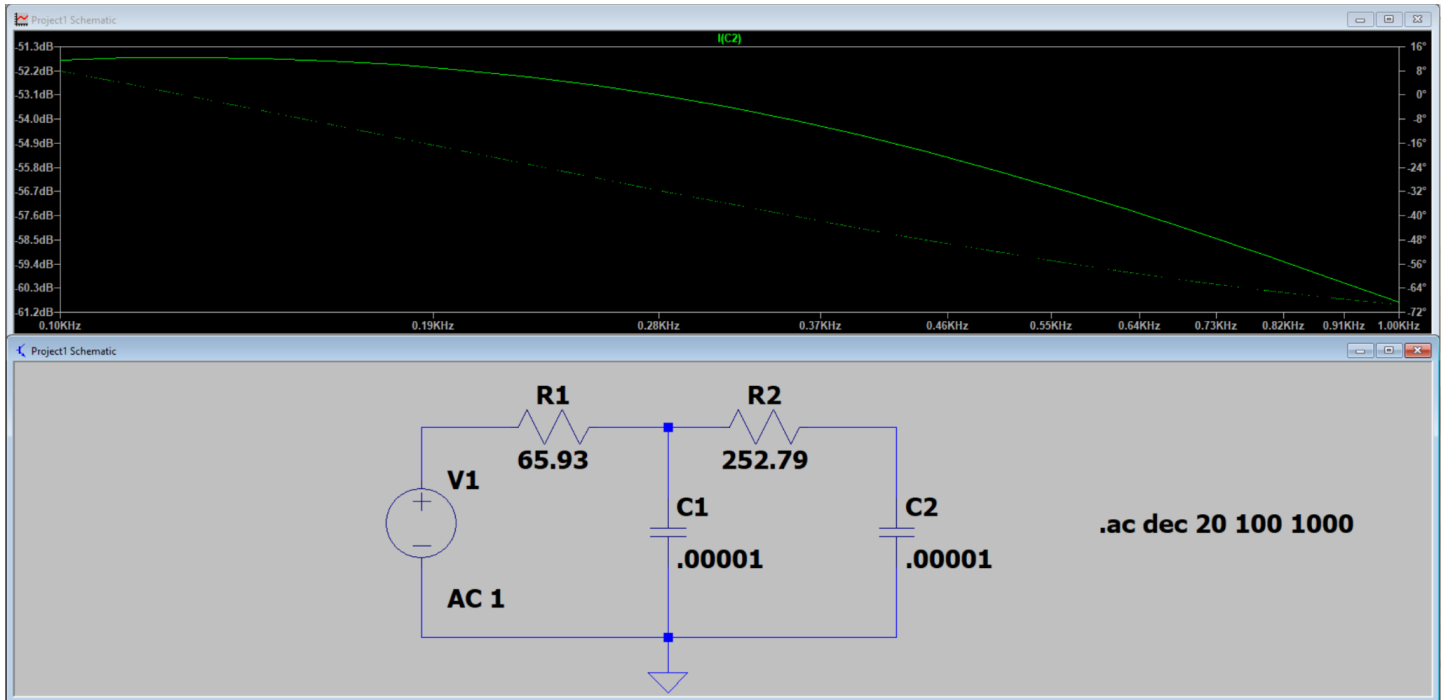

## Problem 5:

### MATLAB Script:

```
close all;
clear all;
clc;

%All Resistor and Capacitor Declarations
R1 = 110;
R2 = 120;
C1 = 10^-6;
C2 = 10^-6;

%Count of graphs being produced.
num = 20;

QX = [R1 R2 C1 C2];

b = [1;0;0];
r = [1 2 3 4 5 6 7 8 9];
w = [r, (10*r), (1e2*r), (1e3*r), (1e4*r), (1e5*r)];
freq = (w/(2*pi));

for s = 1:num
    Q = variation(QX);
    % This function produces random variables of the element values, which are
    % within 20% of the nominal ones.

    G = zeros(3,3); C = zeros(3,3);
    %This line saves us some time, since we now need to enter only the nonzero
    %elements in G and C.

    G(1,1) = 1;
    G(2,1) = -1/Q(1);
    G(2,2) = 1/Q(1);
    G(2,3) = -1/Q(2);
    G(3,2) = -1/Q(2);
    G(3,3) = 1/Q(2);


    C(2,2) = Q(3);
    C(3,3) = Q(4);
    %For each new set of elements values, matrices G, C and L must be
    %recomputed.

    mag = zeros(3,1);
    %vector mag is initialized


    for k = 1: length(w)
        omega = w(k);
        % omega is the next frequency

        A = G+i*omega* C;
        x = A\b;
        %Vector X contains the solution of the node voltage equation in complex
        form
```

### MATLAB Simulation Result:

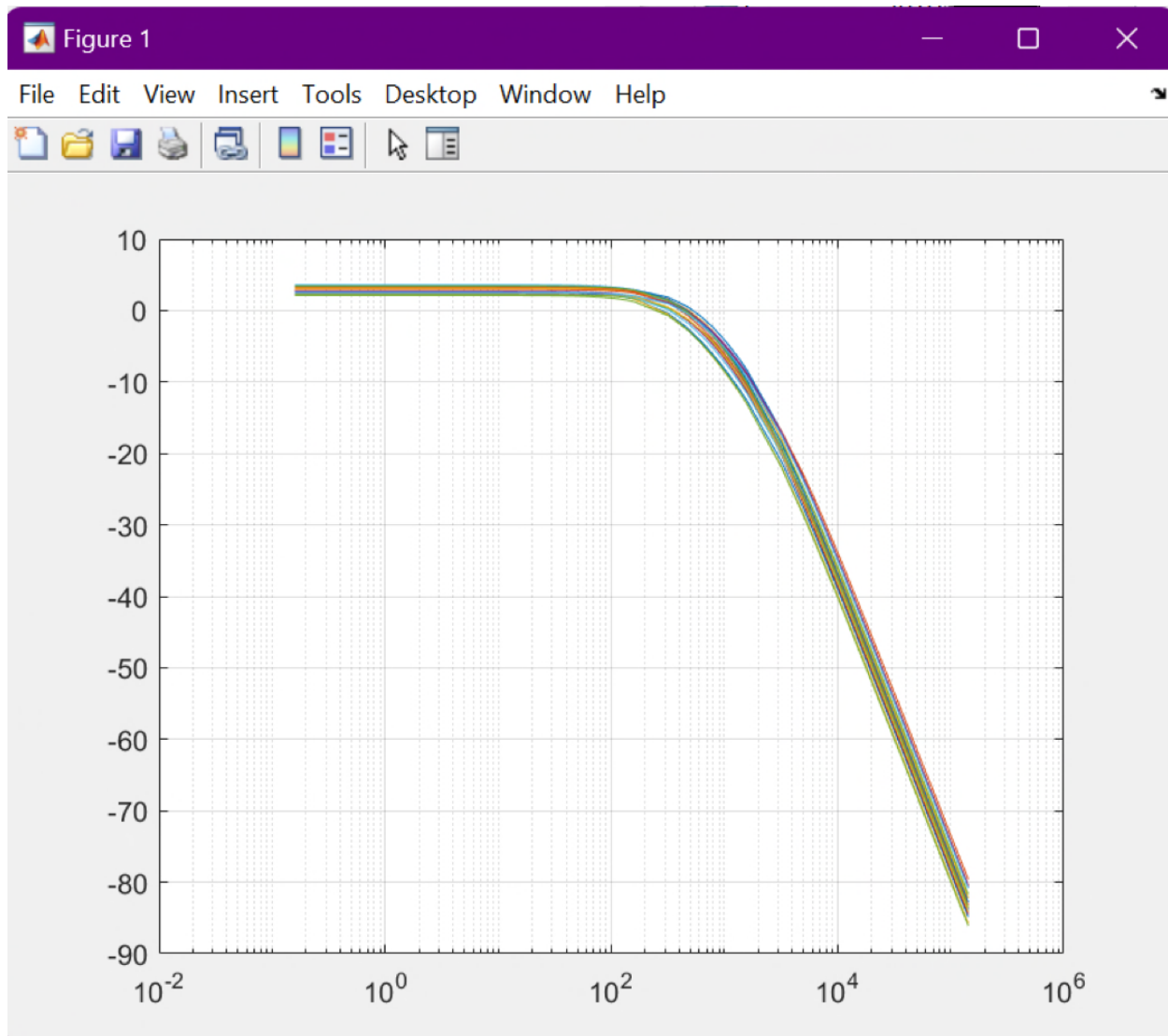

## MATLAB Run-time Results:

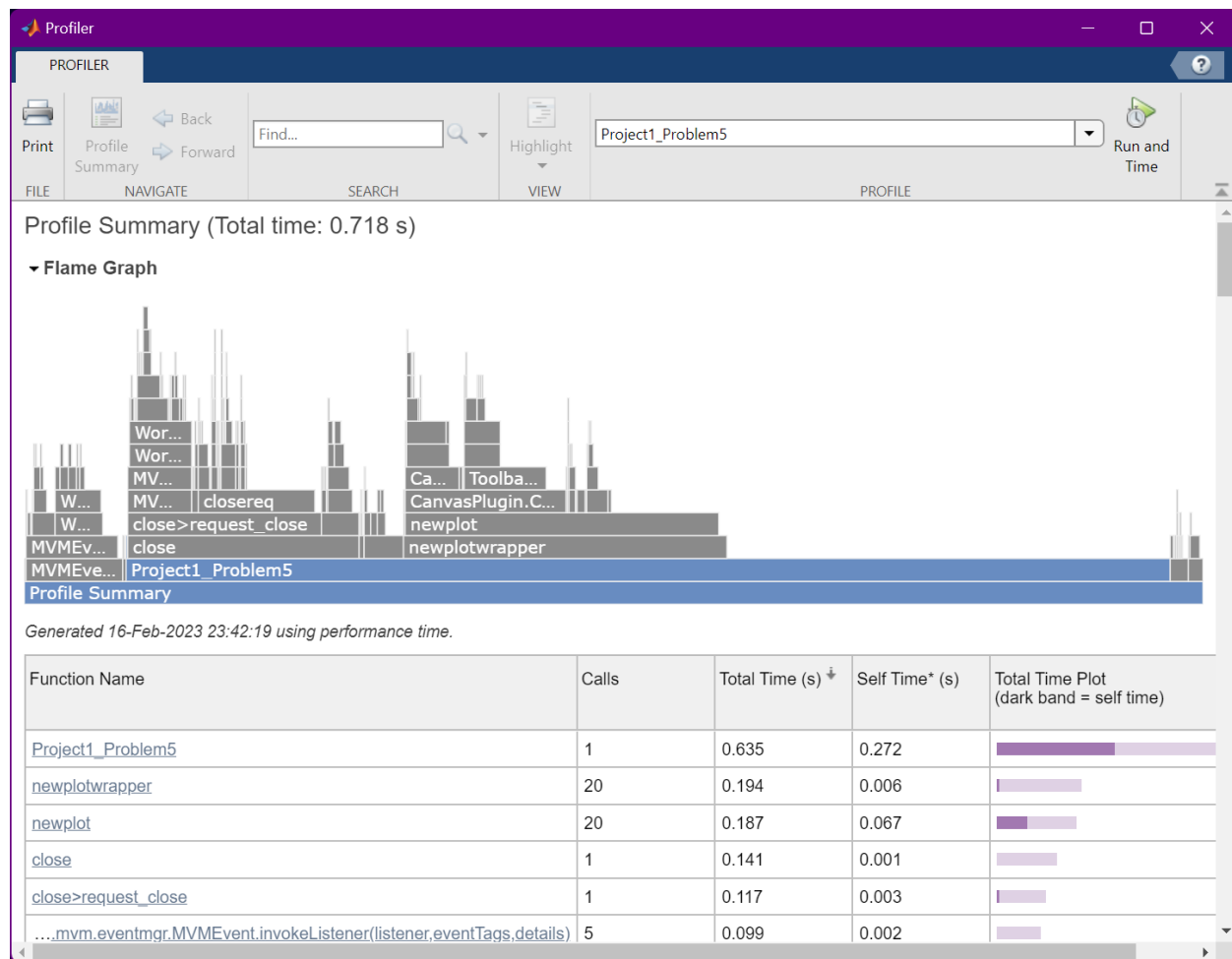

## Problem 6:

### Measured Resistor and Capacitor Values:

R1: .109k

R2: .119k

C1: 96.3nF

C2: 1.035μF

### Measured Results from Assembled Circuit:

#	Frequency	Amplitude	Gain (dB)	Phase (°)				
1	500	1	-1.87	-36.73				
2	596.6	1	-2.45	-41.72				
3	711.8	1	-3.17	-46.98				
4	849.3	1	-4.03	-52.08				
5	1013.4	1	-4.98	-57.1				
6	1209.1	1	-6.08	-61.96				
7	1442.7	1	-7.27	-66.48				
8	1721.4	1	-8.57	-70.65				
9	2053.9	1	-9.91	-74.5				
10	2450.6	1	-11.3	-78.01				
11	2924	1	-12.72	-81.28				
12	3488.8	1	-14.19	-84.36				
13	4162.8	1	-15.68	-87.3				
14	4966.9	1	-17.19	-90.21				
15	5926.3	1	-18.71	-93.13				
16	7071.1	1	-20.3	-96.17				
17	8437	1	-21.9	-99.33				
18	10066.7	1	-23.53	-102.7				
19	12011.2	1	-25.2	-106.35				
20	14331.4	1	-26.96	-110.35				
21	17099.8	1	-28.82	-114.62				
22	20402.9	1	-30.73	-119.23				
23	24344	1	-32.73	-124.04				
24	29046.4	1	-34.87	-129.03				
25	34657.2	1	-37.16	-133.96				
26	41351.9	1	-39.55	-138.83				
27	49339.6	1	-42.16	-143.57				
28	58870.4	1	-44.83	-147.74				
29	70242.2	1	-47.57	-151.65				
30	83810.6	1	-50.46	-155.54				
31	100000	1	-53.42	-159.14				
32	119316.6	1	-56.53	-162.48	47	1687392	1	-59.07 77.43
33	142364.6	1	-59.73	-166.58	48	2013339	1	-57.72 73.65
34	169864.6	1	-62.98	187.67	49	2402249	1	-56.25 76.36
35	202676.8	1	-66.32	180.56	50	2866283	1	-54.63 74.01
36	241827.1	1	-69.68	167	51	3419952	1	-52.96 73.54
37	288540	1	-72.34	148.68	52	4080572	1	-51.31 70.85
38	344276.2	1	-73.78	120.16	53	4868801	1	-49.73 65.37
39	410778.8	1	-72.31	101.21	54	5809289	1	-47.99 61.77
40	490127.4	1	-70.5	92.4	55	6931448	1	-46.12 58.33
41	584803.5	1	-68.92	82.27	56	8270371	1	-44.12 52.19
42	697767.9	1	-67.06	82.89	57	9867929	1	-41.75 45.67
43	832553.2	1	-65.25	79.9	58	11774080	1	-38.91 37.92
44	993374.5	1	-63.66	79.41	59	14048437	1	-35.42 28.25
45	1185261	1	-62.02	78.59	60	16762122	1	-30.12 16.03
46	1414214	1	-60.95	77.46	61	20000000	1	-19.92 -1.32

MATLAB Script:

## Set up the Import Options and import the data

```
opts = delimitedTextImportOptions("NumVariables", 5);

% Specify range and delimiter
opts.DataLines = [2, Inf];
opts.Delimiter = ",";

% Specify column names and types
opts.VariableNames =
    ["VarName1", "FrequencyHz", "AmplitudeVpp", "GaindB", "Phase"];
opts.VariableTypes = ["double", "double", "double", "double", "double"];

% Specify file level properties
opts.ExtraColumnsRule = "ignore";
opts.EmptyLineRule = "read";

% Import the data
MeasuredResults = readtable("C:\Users\purin\Documents\SCU\2022-2023\ELEN
    100\ELEN 100 Lab\ELEN 100 Project 1 Deliverables\Measured Results.csv",
    opts);
```


## Clear temporary variables

```
clear opts


x = MeasuredResults.FrequencyHz;
y = MeasuredResults.GaindB;

semilogx(x,y)
grid
ylabel('20log|H(jw)|');
xlabel('w (rad/sec)');
```

### MATLAB Simulation Result:

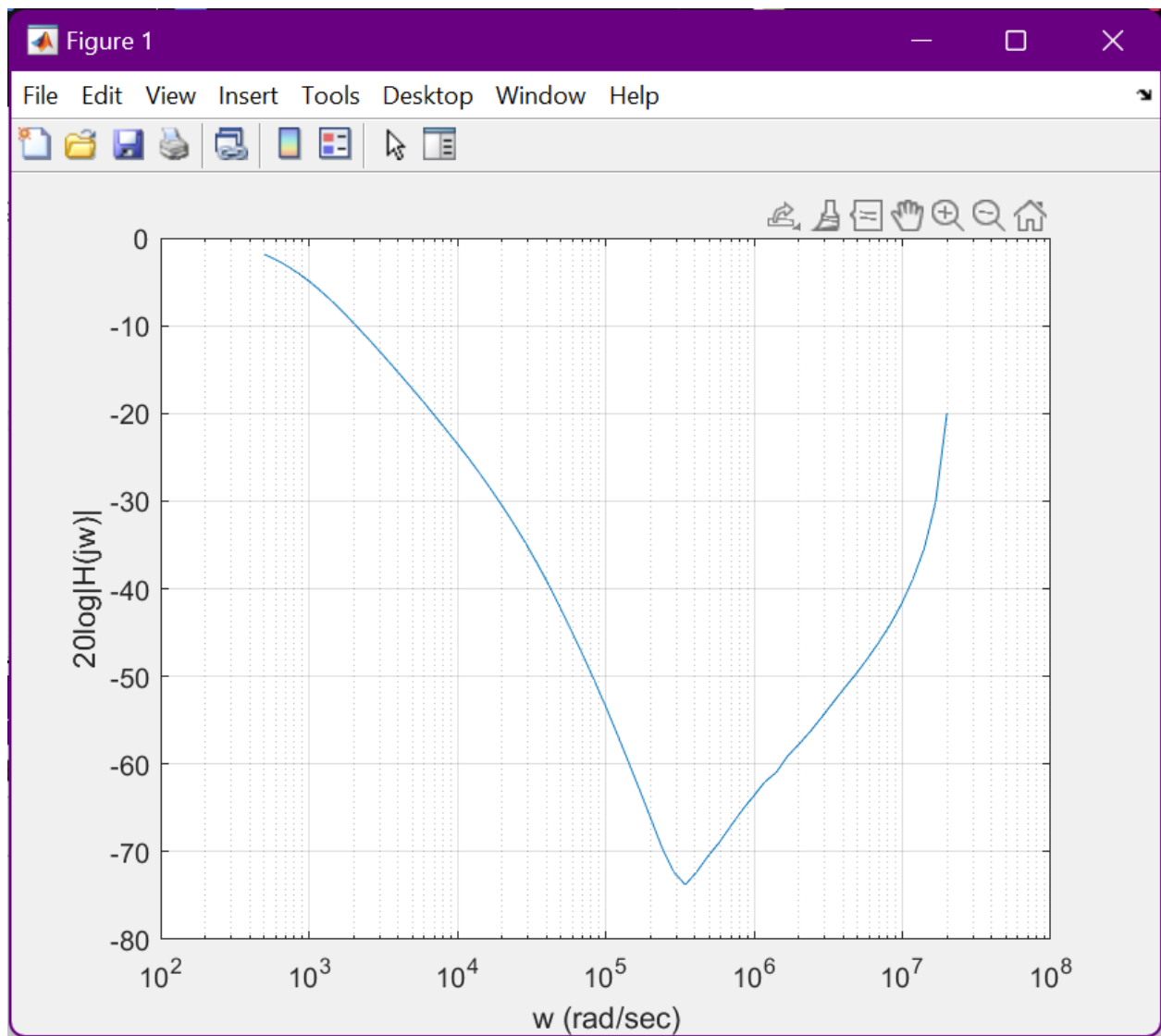


## MATLAB Run-time Results:

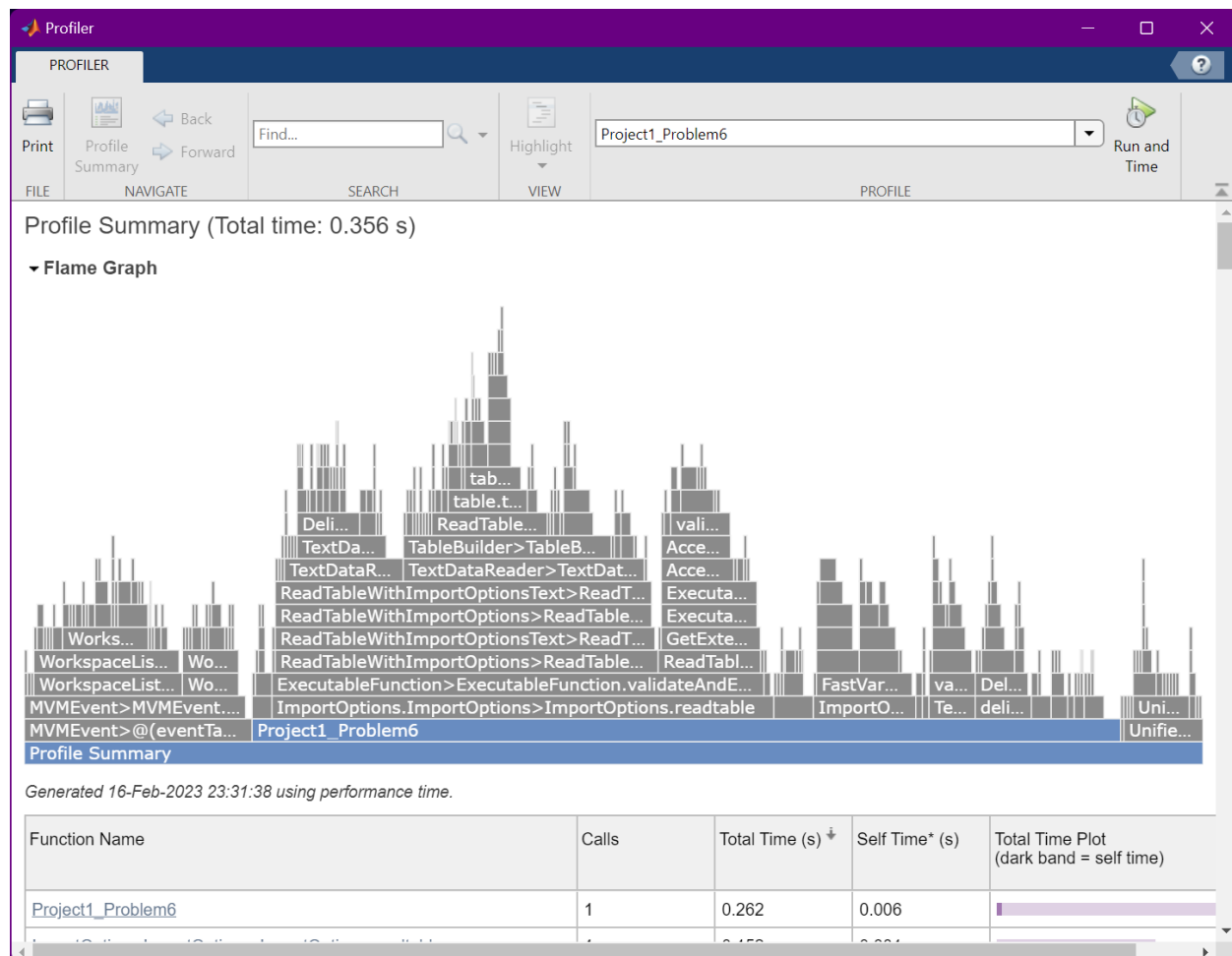


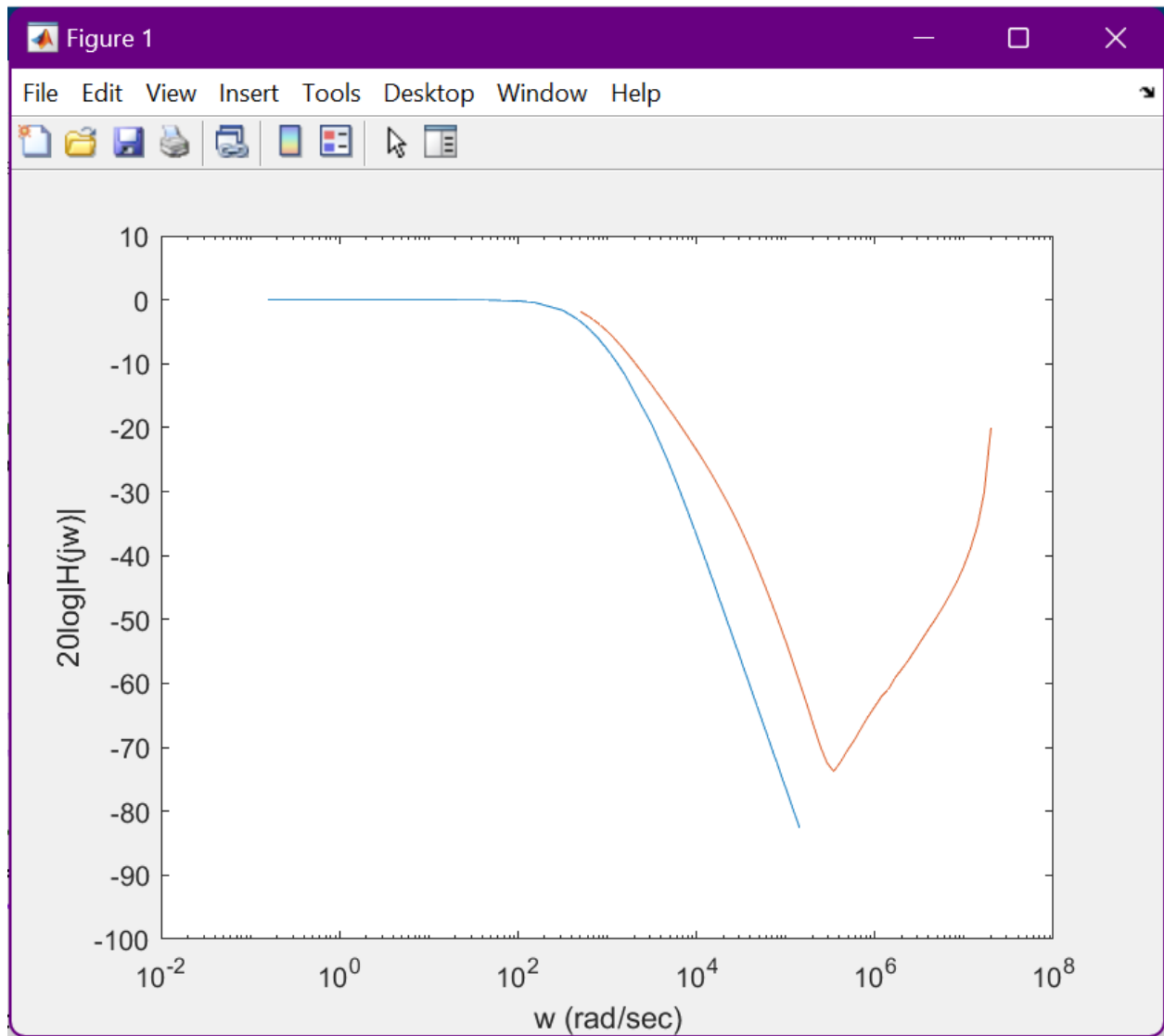
### MATLAB Simulation Compared to Problem 3:



### MATLAB Simulation Compared to Problem 5:

